

Implementation and Simulation Results




- The design is implemented using 90 nm Technology in Cadence using gpdk90 library
- The width and lengths are taken as per the specifications given in the paper
- Beside table shows the lengths and width Of the various mosfets used in the circuit


MOSFET	W/L(SIZE)
M1	3μ/500nm
M2	3μ/500nm
M3	7μ/500nm
M4	7μ/500nm
M5	6μ/500nm
M6	30μ/500nm
M7	30μ/500nm
M8	6μ/500nm
M9	6μ/500nm
C _L	3pF
C _c	680fF

Single stage


Schematic diagram:

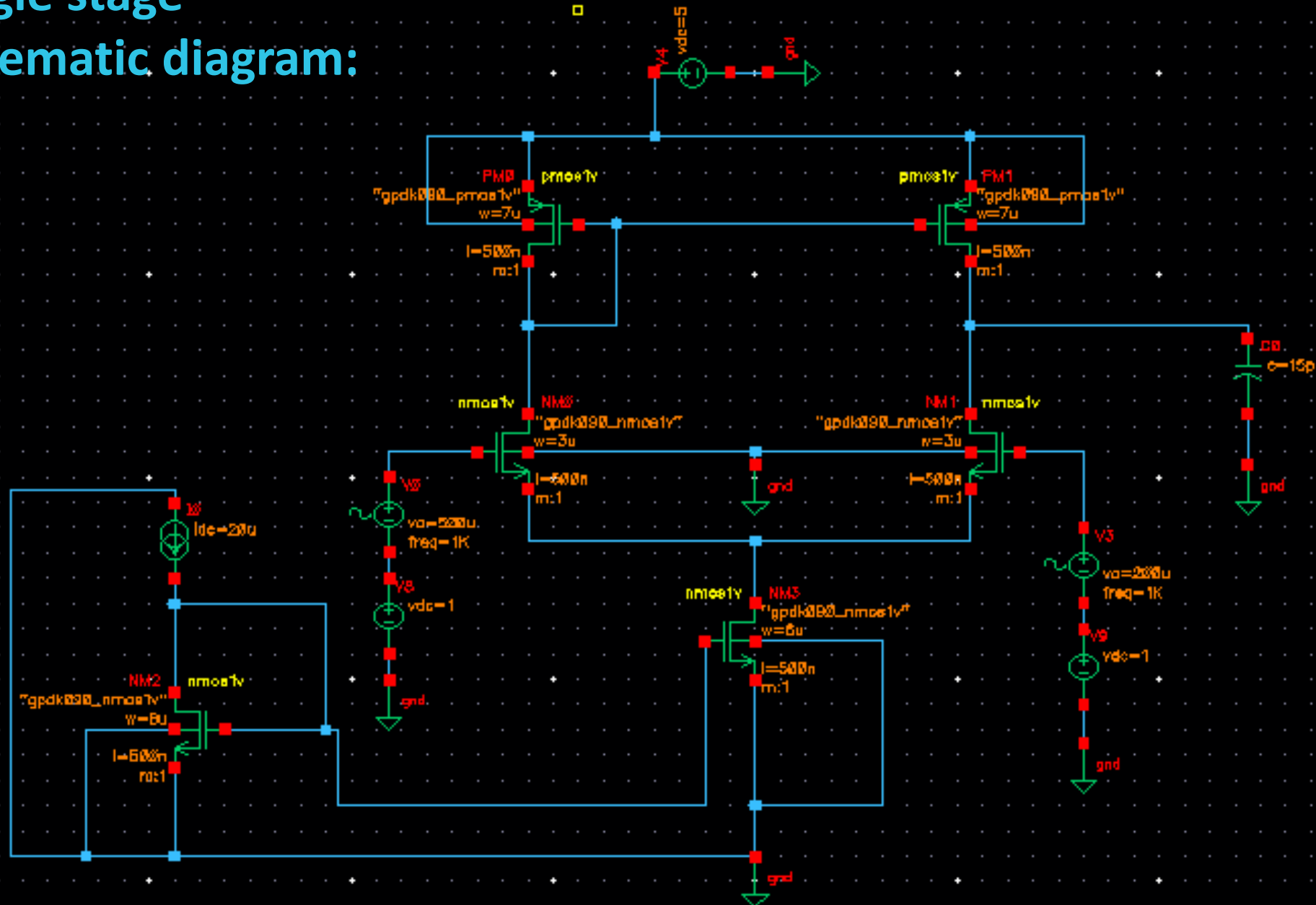


Input and Output waveforms:

 

Two stage Schematic diagram:

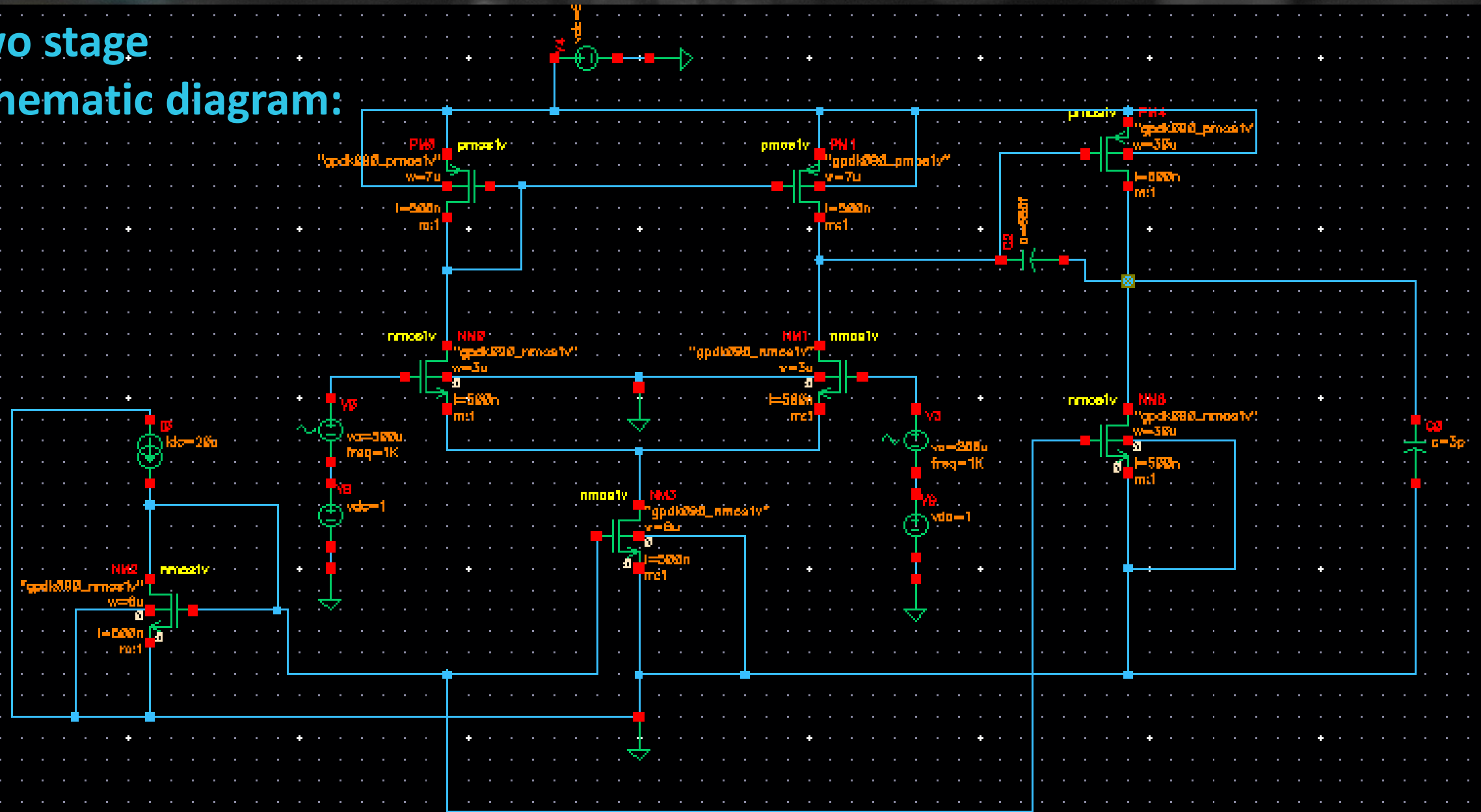

Input and Output waveforms:

 

Gain and CMRR Calculations



Differential mode:

$$V1 = 1 \text{ mV pk-pk } 1\text{kHz}$$

$$V2 = 0.4 \text{ mV pk-pk } 1\text{kHz}$$

$$V_{in} = V1 - V2$$

$$= 0.6 \text{ mV pk-pk}$$

$$V_{out} = 664 \text{ mV pk-pk (from the graph)}$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{664}{0.6} = 1106$$

$$\text{Gain in dB} = 20\log_{10} 1106 = 60.88 \text{ dB}$$

$$\text{CMRR} = \frac{A_d}{A_c} = \frac{1106}{0.2} = 5530$$

$$\text{CMRR in dB} = 74.8 \text{ dB}$$

common mode:

$$V1 = 1 \text{ mV pk-pk } 1\text{kHz}$$

$$V2 = 1 \text{ mV pk-pk } 1\text{kHz}$$

$$V_{in} = \frac{V1 + V2}{2}$$

$$= 1 \text{ mV pk-pk}$$

$$V_{out} = 0.2 \text{ mV pk-pk (from the graph)}$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{0.2}{1} = 0.2$$

$$\text{Gain in dB} = 20\log_{10} 0.2 = -14 \text{ dB}$$

Conclusion



The two stage operational amplifier was simulated in cadence with gpdk90nm technology.

After simulating the proposed circuit we have got high gain of 61dB with several other good parameters. CMRR of 75dB . the response of the circuit is very high as a result its gets an edge over other circuits and the CMRR with the proposed technique increases its value.