

PROPOSED TECHNIQUE



We know that $CMRR = \frac{A_d}{A_c}$

A_d → differential gain

A_c → common mode gain

CMRR can be increased by $\uparrow A_d$ and $A_c \downarrow$

→ A_d is increased by using two stages

→ A_c is decreased by increasing the R_{DS} of mosfet as

$$A_c = \frac{1}{2R_{DS}}$$

→ R_{DS} is increased by using another mosfet as resistor

→ A capacitor is connected between output of stages and input of stage 2 for miller compensation to increase phase margin

The circuit is modelled as


Cont..



MILLER EFFECT:

By using small 'C' we can get larger value of 'C' by miller effect.

- It is used for better phase margin. If p_1 (pole 1) can be shifted towards left and p_2 (pole 2) can be shifted towards right then phase margin will be better. As we can see in the diagram above the effect of capacitance "C" in pole P_1 & P_2 , by implementing in P_1 the pole shifts greatly towards left and P_2 shifts towards right. So here miller capacitor is being used to get good phase margin.

 

Cont..

*The proposed
circuit diagram:*

